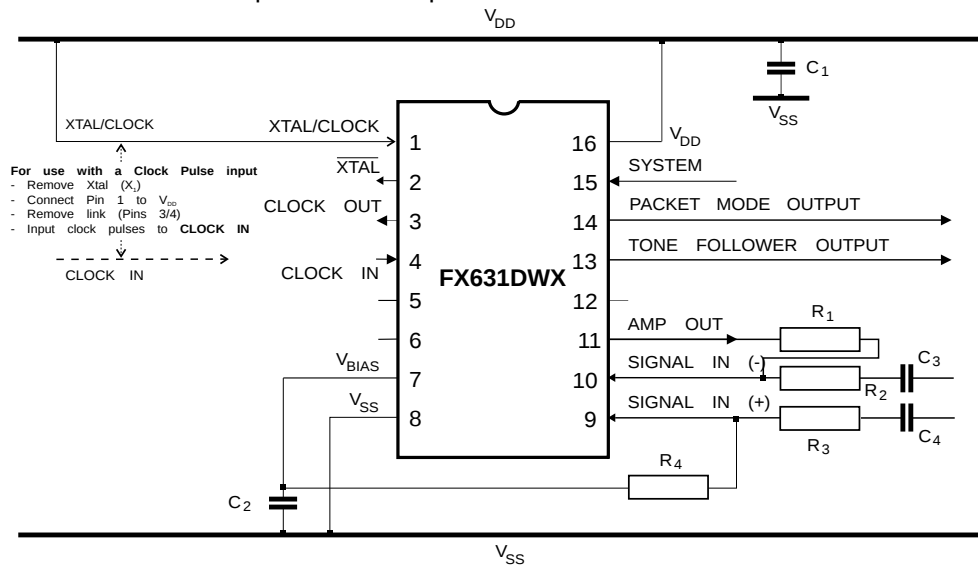


FX631xxX Clocking Options


Introduction

This device is function and pin-compatible with the current FX631 devices. However please note that this particular product will only operate under one of the following conditions, as illustrated in the diagrams below:

- 1 For customers who do not require the on-chip oscillator and who have an external clock available.



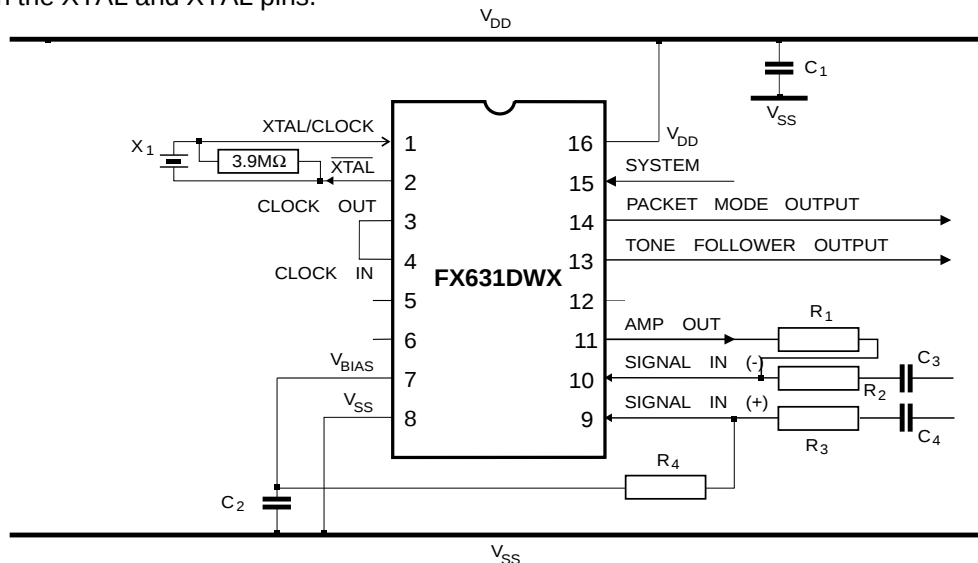- 2 For correct operation using the on-chip Xtal oscillator, a 3.9Meg-Ohm resistor should be connected between the XTAL and XTAL pins.



Product Types Affected:

FX631DWX

FX631PX

Note that this Application Note is intended to be used in conjunction with the current CML Product Data Sheet; printed Specifications apply.
CML does not assume any responsibility for the use of any circuitry described. No circuit patent licences are implied
and CML reserves the right at any time without notice to change the said circuitry.



CONSUMER MICROCIRCUITS LIMITED
1 WHEATON ROAD - WITHAM - ESSEX CM8 3TD - ENGLAND
© 1997 Consumer Microcircuits Limited

Telephone: +44 1376 513833
Telefax: +44 1376 518247
e-mail: sales@cmlmicro.co.uk
<http://www.cmlmicro.co.uk>